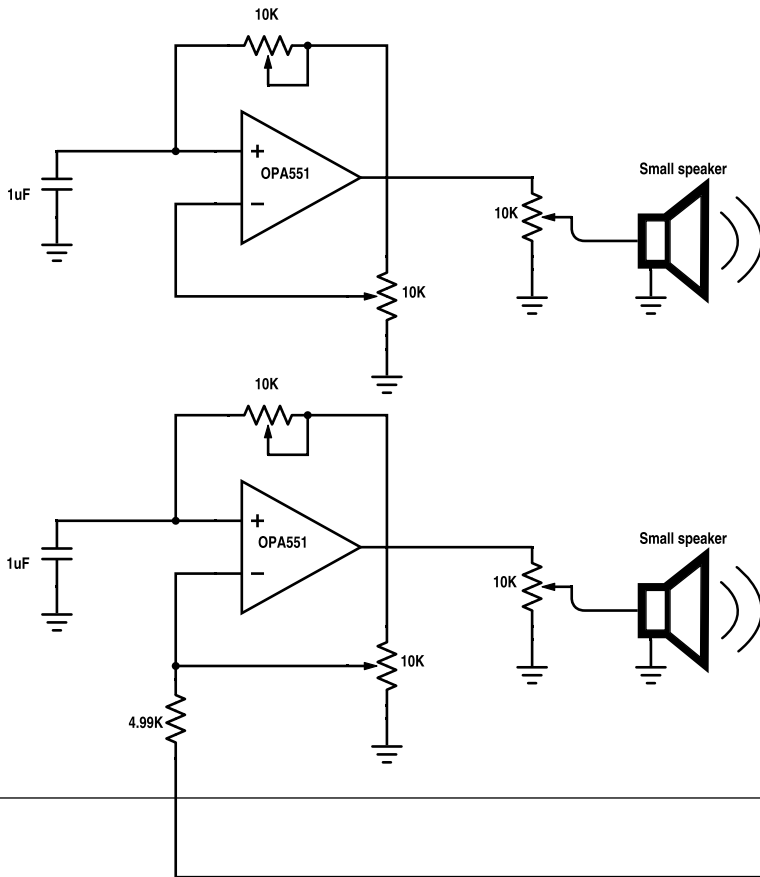


Place the two oscillator circuits on the same breadboard to induce synchronization through parasitic capacitance.



Oscillator frequency in demo: 2000 Hz

